

1 - Binary and logic

Eric Mayhew & Jacob Errington

This lesson provides its participants with an introduction to circuits and binary. Understanding binary and circuits are at the soul of computers, therefore it is essential they are discussed in order to be comfortable with computers. By implementing logic gates using breadboards, participants will learn how basic circuits are constructed using hands-on learning activities. Understanding circuitry will lay the ground work for introducing more complicated concepts like integrated circuits and processors in later lessons.

Overview

Lesson Objectives

By the end of the lesson, students will be able to:

- Explain the function of the power supply unit in the computer.
- Build basic logic gates out of transistors, both theoretically and physically on a breadboard.
- Name a few basic Haskell types and use an interactive Haskell prompt like GHCi.

Materials

To run this lesson, the following are needed:

- lesson slides;
<https://www.computing-workshop.com/pdf/1-presentation.pdf>
- one breadboard for each group and enough of the following electronic components: NPN transistors, 10 Ω resistors, 9 V batteries, 5 V voltage regulators, jumper wires (male to male), and assorted LEDs.

Instructional Sequence

5 mins. Facilitators welcome the group and present lesson agenda.

25 mins. Using the slides, facilitators will present the power supply unit, which turns alternating current to direct current, a form of electricity computers can use. To represent this, students will implement a basic circuit on their breadboard.

Before creating the circuit, facilitators will explain the purpose of each component using the slides.

The students will now create the circuit shown on slide 10. Building this circuit will require: the breadboard, a resistor, voltage regulator (VR), the battery, and a LED. The circuit will run a current through the VR, then the LED, then a resistor and back to the batter. The LED light will to turn it on, demonstrating a basic circuit. Students should add a button anywhere before the LED on their circuit to get familiar with its function.

20 mins. Once students feel comfortable with using the breadboard to create circuits, facilitators will introduce transistors. For our purpose, transistors act as electronic switches which are used to manipulate binary values.

Students will add a transistor to their breadboard. They will do this by moving the output of the LED current into the base (middle prong) of the transistor. Then they will connect the collector (left prong) to a different colour LED and to the positive voltage. Finally the emitter (right prong) will connect to the negative voltage.

Pressing the button of the base wire will light up both the base LED and collector LED. Explain this is because the base makes the transistor conductive, allowing electricity to move from collector to emitter. The base is like a spigot on a tap: when it is open, water flows; when it is closed, water does not flow.

35 mins. When students are comfortable with transistors, they will use 2 transistors to make the "and" & "or" logic gate. To create an and gate using transistors, refer to this video: <https://www.youtube.com/watch?v=sTu3LwpF6XI&t=488s>.

10 mins. The rest of the class will introduce Haskell and programming languages. To tie in pre-existing knowledge of hardware, students will understand compilation to be moving down the latter of abstraction. Participants are now prepared to complete the www.tryhaskell.org by the next session.

Homework

Students should build an intuitive understanding of Haskell syntax and types by completing www.tryhaskell.org up to but not including lesson 4 (on pattern matching).